

5. 2N7000 and Active Buzzer

2N7000 pins

Verify Gate/Drain/Source against the datasheet for your exact transistor.

Gate -> GPIO18 through 220 ohm

Gate -> GND through 100 kohm

Source -> GND

Drain -> buzzer negative (-)

Buzzer

Buzzer positive (+) -> +5V

Buzzer negative (-) -> MOSFET drain

Use an active 5V buzzer.